



Discrete Semantics for Reversible Transistor Network Verification

Hannah Blyton and Hugh Potter · RC 2026

Two kinds of chip bug



Pentium FDIV: logical bug

- The implemented arithmetic did not match the intended digital behaviour.



Z80 ED-71: floating bus

- An undefined instruction samples an electrically floating internal bus.

How we prevent them

- ▶ **Formal verification:** assertions, model checking, equivalence checking, STE, SMT, and theorem proving for RTL and above
- ▶ **Electrical rule checking:** foundry and PDK rules over extracted netlists, including shorts, floating nodes, drive strength, and conduction cases
- ▶ **Simulation:** RTL, gate-level, switch-level, and analogue simulation, each at a different abstraction boundary
- ▶ **Silicon testing:** process corners, voltage and temperature corners, burn-in, ageing, noise, power integrity, and long-run stress

DSRT

Adiabatic switching rules are electrical rules, not logical rules.

We want formal verification at the switch level
for adiabatic transistor networks.

DSRT: Machine-checked semantics for adiabatic switching

- ▶ Electrical adiabaticity constraints formalised in Lean.
- ▶ Logical reversibility comes as a corollary of constraints.
- ▶ Definitions support machine-checked proofs on circuit behaviour.
- ▶ Enables easier switch-level reasoning.

DSRT: Applications


- ▶ `dsrt-sim`: a verified timestep simulator
 - ▶ Simple timestep simulation relation: adiabaticity forbids switching cascades, avoiding the cycle resolution required for traditional switch-level simulation.
 $O(t + n)$
 - ▶ Verified correct in forward and reverse directions.
 - ▶ Python + Rust simulator implementations.
- ▶ Verification of new logic families
- ▶ Verification of compiler output

Adiabatic switching rules

- (0) No active shorts.
 - 1. Avoid the use of diodes.
 - 2. Allow voltages to change only via slow, linear ramps.
 - 3. Avoid turning a transistor on when its source and drain are at different voltages (no sparks).
 - 4. Avoid turning a transistor off while current is passing through it, unless there is an alternate low-impedance path (no squelches).

Frank et al. [1]

(0) No active shorts

 


$$CON(S) \iff \nexists 0 \rightsquigarrow_S 1$$

No conductive path may join a node driven to 1 with one driven to 0.

CON is the baseline well-formedness condition before any adiabatic handoff is considered.

1. Avoid the use of diodes

 


Forward voltage drop
energy dissipated as heat

$$P_{\text{dissipated}} = V_D I$$

A conducting diode's built-in voltage drop prevents fully adiabatic charge recovery.

1. Avoid the use of diodes

 


Forward voltage drop
energy dissipated as heat

$$P_{\text{dissipated}} = V_D I$$


DSRT networks do not contain diodes; they are excluded by construction.

 2. Allow voltages to change only via slow, linear ramps



$$E_{\text{loss}} = \frac{1}{2} CV_{DD}^2$$

Per charging event

 


$$E_{\text{loss}} \approx \frac{RC}{\tau} CV_{DD}^2$$

Vanishes as $\tau/RC \rightarrow \infty$

Athas et al. [2]

 2. Allow voltages to change only via slow, linear ramps




The low/rising/high/falling four-phase waveform is implicit, while the transition relation checks one two-state window (A, B) at a time.

3. Avoid turning a transistor on when its source and drain are at different voltages (no sparks)

Allowed


Gate unchanged

 

The transistor stays off;
no conducting path
appears.

Allowed


*Gate changes; endpoints
agree*

 

The transistor turns on
across zero voltage
difference.

Not allowed


*Gate changes; endpoints
disagree*

 


Turning the transistor on
forces unequal voltages to
equalise.

3. Avoid turning a transistor on when its source and drain are at different voltages (no sparks)


Allowed

 

Allowed

 

Not allowed

 



3. Avoid turning a transistor on when its source and drain are at different voltages (no sparks)

For every transistor t , with gate g_t , source s_t , and drain d_t :

$$ADB(A, B) \iff \forall t, A(g_t) \neq B(g_t) \implies (A(s_t) = A(d_t)) \wedge (B(s_t) = B(d_t)).$$

“For every transistor, if its gate changes between state A and state B , then its source and drain must already agree in state A , and they must also agree in state B .”

  4. Avoid turning a transistor off while current is passing through it, unless there is an alternate low-impedance path (no squelches)



Both rails ride one rising ramp and the gates share V_{in} . As V_{in} falls, the output hands off from the NMOS to the PMOS path; V_{out} tracks the ramp, so source and drain agree – no spark, *ADB holds*. But if the NMOS opens before the PMOS closes, V_{out} loses all power mid-current: a squelch, *PTC fails*.

4. Avoid turning a transistor off while current is passing through it, unless there is an alternate low-impedance path (no squelches)


For every node v :

$$PTC(A, B) \iff \forall v, A(v) \neq B(v) \implies (\exists p, \text{powered}_A(p) \wedge v \leftrightarrow_A p \wedge v \leftrightarrow_B p) \\ \wedge (\exists q, \text{powered}_B(q) \wedge v \leftrightarrow_A q \wedge v \leftrightarrow_B q).$$

“If a node changes between state A and state B , then it must have a persistent conductive path to an A -powered node, and also to a B -powered node.”

CLEAN: Don't charge to weak values

optional

 

Node X is charged by a PMOS; node Y is charged by an NMOS.

CLEAN: Don't charge to weak values

optional


For every node v :

$$CLEAN(A, B) \iff \forall v, B(v) = 0 \vee B(v) = 1.$$

“Every sampled node in state B must have a strong value: either 0 or 1, not a degraded low or degraded high.”

STAT: Do not rely on a floating node staying put

optional

 

The discrete state records $x = 1$ throughout, but once the driver disconnects, the real node floats and drifts. Reconnecting to the 1 driver snaps it back through an uncontrolled current spike – a spark.

STAT rules this out by requiring every node to keep a strong path to a powered node, so reconnection can never conceal a short.

STAT: Do not rely on a floating node staying put

optional

For every node v :

$$STAT(A, B) \iff \forall v, \exists p, \text{powered}_B(p) \wedge v \leftrightarrow_B p.$$

“Every node in state B must be connected, through transistors that are on in B , to some node powered in state B .”

The five constraints at a glance

Constraints on state B

CON Connected nodes have the same value.

CLEAN Every sampled value is strong: 0 or 1.

OPTIONAL

STAT Every node has a strong path to a node powered in B .

OPTIONAL

Constraints on transition (A, B)

ADB If a transistor gate changes, its source and drain agree in both A and B .

PTC Every changed node has a strong, persistent path to powered nodes in both A and B .

A valid DSRT step satisfies $CON \wedge ADB \wedge PTC$, with $CLEAN \wedge STAT$ optionally enforced.

Two useful consequences

$$CON(B) \wedge ADB(A, B) \wedge PTC(A, B) \implies DDC(A, B) \wedge CAP(A, B)$$

DDC

Nodes cut off from the B -powered components have the same values in A and B .

CAP

Nodes A -connected to a B -powered component have its logical value in B .

This way of classifying nodes helps us reason about both simulation and logical reversibility.

DDC: Disconnected nodes do not change

$$DDC(A, B) \iff \forall v, \left(\forall p, \text{powered}_B(p) \Rightarrow v \leftrightarrow_A^{\text{strong}} p \right) \Rightarrow A(v) = B(v).$$

If a node cannot be reached from any B -powered node, using strong connections in A , then it has the same value in A and B .

Intuition: *PTC* says every changed node must have a persistent path to powered nodes. So if there is no path to a B -powered node, the node cannot have changed.

CAP: Connected nodes take the powered value

$$CAP(A, B) \iff \forall v, p, (v \leftrightarrow_A p \wedge \text{powered}_B(p)) \Rightarrow \text{logic}(B(v)) = \text{logic}(B(p)).$$

If a node is connected in A to a node powered in B , then they have the same logical value in B .

Intuition: Walk along the connection path in A . Each transistor either stays on, so $CON(B)$ keeps the endpoints equal, or switches off, so ADB says the endpoints already agree in B .

Logical reversibility

For a transition relation R , logical reversibility means uniqueness in both directions:

$$R(A, B) \wedge R(A, C) \Rightarrow B = C$$

$$R(B, A) \wedge R(C, A) \Rightarrow B = C$$


With the same powered assignment fixed, can two different electrical assignments both satisfy

$$CON \wedge ADB \wedge PTC \wedge CLEAN$$


for the same tick?

Every node is forced

 Pick any node v . Look at the A -connectivity between v and the nodes powered in the next state.


 
$$CAP(A, B) : \\ \text{logic}(B(v)) = \text{logic}(B(p)).$$



$$DDC(A, B) : \\ B(v) = A(v).$$

Every node is forced

$$CON \wedge ADB \wedge PTC \implies DDC \wedge CAP$$

Connected in A

Disconnected in A

$$CAP(A, B)$$

$$DDC(A, B)$$

$\implies$ v takes the powered value
therefore uniquely determined

$\implies$ v keeps its old value
therefore uniquely determined

Backward determinism

Forward view

$$A + \text{powered}_B \Rightarrow B$$

$$\begin{array}{l} \text{CON}(A) \\ \text{ADB}(A, B) \\ \text{PTC}(A, B) \end{array} \Rightarrow \begin{array}{l} \text{DDC}(A, B) \\ \text{CAP}(A, B) \end{array}$$

Backward view


$$B + \text{powered}_A \Rightarrow A$$

$$\begin{array}{l} \text{CON}(B) \\ \text{ADB}(B, A) \\ \text{PTC}(B, A) \end{array} \Rightarrow \begin{array}{l} \text{DDC}(B, A) \\ \text{CAP}(B, A) \end{array}$$

$$\text{ADB}(A, B) \iff \text{ADB}(B, A), \quad \text{PTC}(A, B) \iff \text{PTC}(B, A).$$

Backward uniqueness is the same local forcing argument, with the two endpoints renamed.

Aside: Transistors and if statements

 

Same cascade as code



```
if x:
    b := a
    if b:
        c := a
```

The second guard reads b after the first assignment.

Ordinary switch-level evaluation may cascade inside one tick.

Aside: Where reversibility breaks

  Instantaneous cascade for `if x: b := a; if b: c := a`



Why simulation becomes simple

DDC and CAP turn the semantic question into reachability.

Reached from power in B

Not reached

A -connected to a powered node

no A -path to power in B

$\Rightarrow$ take that powered value

$\Rightarrow$ keep the old value

This collapse fails for ordinary irreversible gates: the output can be driven by a path whose controlling gate changes in the same tick.

The simulator

```

open := powered nodes;  all others := unknown
# connected nodes share a value  [CAP]
while open not empty:
    near := pop[open]
    for each on-transistor near -> far:
        drive far;  conflict => short circuit
# unknowns keep their previous value  [DDC]
for each node still unknown:
    node := its value in A
# validate, else: no adiabatic successor
check CON, ADB, PTC, CLEAN

```

The simulator – full algorithm for reference

```

1:  $open \leftarrow \emptyset$ ;  $changed \leftarrow \emptyset$ 
2: for each node  $v$  do
3:   if  $v$  is powered in  $B$  then
4:      $B(v) \leftarrow$  powered value of  $v$ ; add  $v$  to  $open$ 
5:   else
6:      $B(v) \leftarrow$  unknown

```

▷ Initialise: set powered nodes, mark rest unknown

```

7: while  $open \neq \emptyset$  do
8:   remove some node  $near$  from  $open$ 
9:   for each transistor  $T$  with endpoint  $near$  and other endpoint  $far$  do
10:    if  $T$  is off in  $A$  then continue
11:     $drive \leftarrow \text{PASS}(\text{type}(T), B(near))$ 
12:    if  $B(far) = \text{unknown}$  then
13:       $B(far) \leftarrow drive$ ; add  $far$  to  $open$  and  $changed$ 
14:    else if  $\text{LOGIC}(B(far)) \neq \text{LOGIC}(drive)$  then
15:      error: short circuit at  $far$ 
16:    else
17:       $B(far) \leftarrow \text{STRONGER}(B(far), drive)$ 

```

▷ Flood-fill from powered nodes using A -connectivity (CAP)

```

18: for each node  $v$  with  $B(v) = \text{unknown}$  do
19:    $B(v) \leftarrow A(v)$ 

```

▷ Set unknowns to previous value (DDC)

▷ Validation: check CON , ADB , PTC , $CLEAN$


Conclusions

DSRT: machine-checked semantics for adiabatic switching.

- ▶ Electrical adiabaticity constraints formalised in Lean; logical reversibility comes as a corollary.
- ▶ Definitions support machine-checked proofs on circuit behaviour.
- ▶ Simple timestep simulation relation – adiabaticity forbids switching cascades, so no cycle resolution needed. $O(t + n)$
- ▶ Verified simulator, correct in forward and reverse directions; Python + Rust implementations.

 Questions?

Flood fill by hand: A ramp and a stored bit



Initial worklist


$open = \{inp, ctrl, ctrl_n, hold\}$
 $seen = \{inp, ctrl, ctrl_n, hold\}$

Known assignments

$B(inp) = 1, B(hold) = 0$
 $B(ctrl) = 1, B(ctrl_n) = 0$
 $B(out) = ?, B(mem) = ?$

State A: $inp = 0, out = 0$, and a stored bit $mem = 1$.
 Powered for B: inp ramps to 1; all gates held.

 Flood fill by hand: DDC – *mem* keeps its bit



Unreached $\Rightarrow$ disconnected in $A \Rightarrow$ the old value stands: *mem* is remembered, not recomputed.


DDC

$B(mem)$ is still unknown
 $B(mem) := A(mem) = 1$

Validate

$CON, ADB, PTC, CLEAN$
 all hold
 $\Rightarrow$ unique adiabatic successor

 Flood fill by hand: Colliding fills are shorts



State A : $a = mid = b = 0$; both gates on, held in B .
 Powered for B : a ramps to 1 while b is held at 0.

Flood fill

pop a : $pass_P(1) = 1 \Rightarrow$
 $B(mid) = 1$

pop b : $pass_N(0) = 0$: conflict!

Short circuit

logic 1 meets logic 0 at mid
 no state B can satisfy CON
 halt and report

Rule (0) – no active shorts – enforced mechanically, for free.

References I

- [1] [Michael P. Frank et al.](#) "Reversible Computing with Fast, Fully Static, Fully Adiabatic CMOS". In: *2020 International Conference on Rebooting Computing (ICRC)*. IEEE Computer Society, 2020, pp. 1–8. DOI: [10.1109/ICRC2020.2020.00014](#).
- [2] [W. C. Athas et al.](#) "Low-Power Digital Systems Based on Adiabatic-Switching Principles". In: *IEEE Transactions on Very Large Scale Integration (VLSI) Systems* 2.4 (1994), pp. 398–407. DOI: [10.1109/92.335009](#).